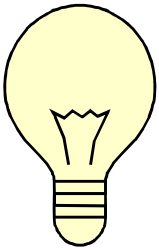


Making Circuits



Materials:
1 battery
2 light bulbs
Insulated Wire
Paper Clips



1. Using the available materials, experiment to light the bulb.
2. Once you light your bulb, draw a "schematic" of your circuit. Use the following conventional symbols for drawing your circuit.



3. See how many different ways can you get the bulb to light? Draw the different ways to light the bulb.

